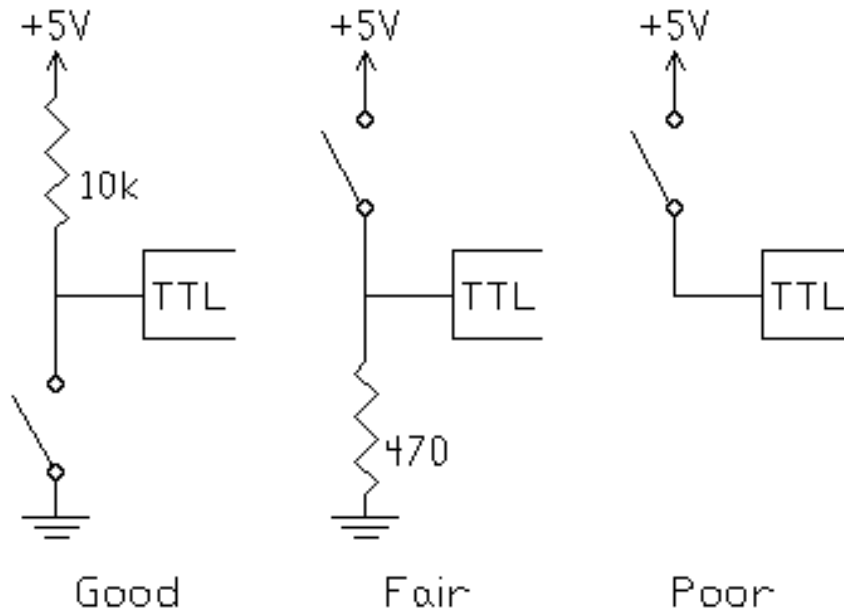


Switches



Quelle: <http://www.freewebs.com/maheshwankhede/ports.html>

- Pullup-Resistor probably provided in uC

Debouncing



- Capacitor
- Code

- waiting

```
if (KEY1_Get()) {  
    WAIT1_Waitms(50); /* simple debounce */  
    if (KEY1_Get()) { /* still pressed? */  
        ...  
    }  
}
```


- Edge detection

uC configuration

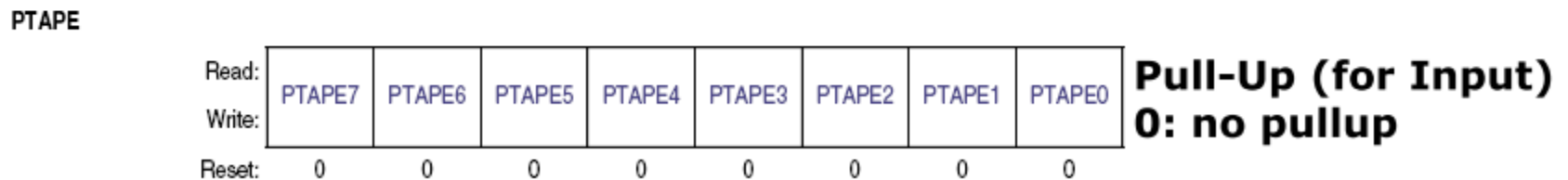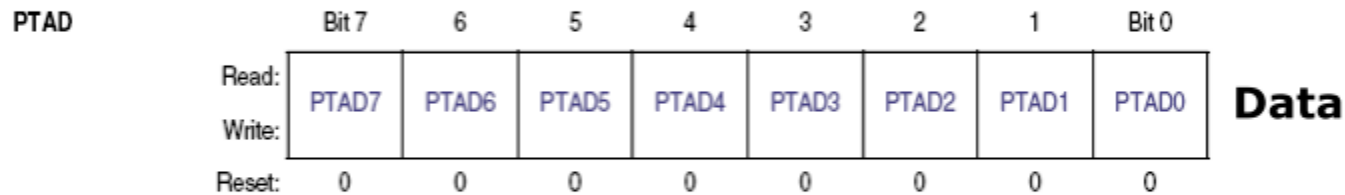

➔ **Processor Expert**


Switches with Interrupts

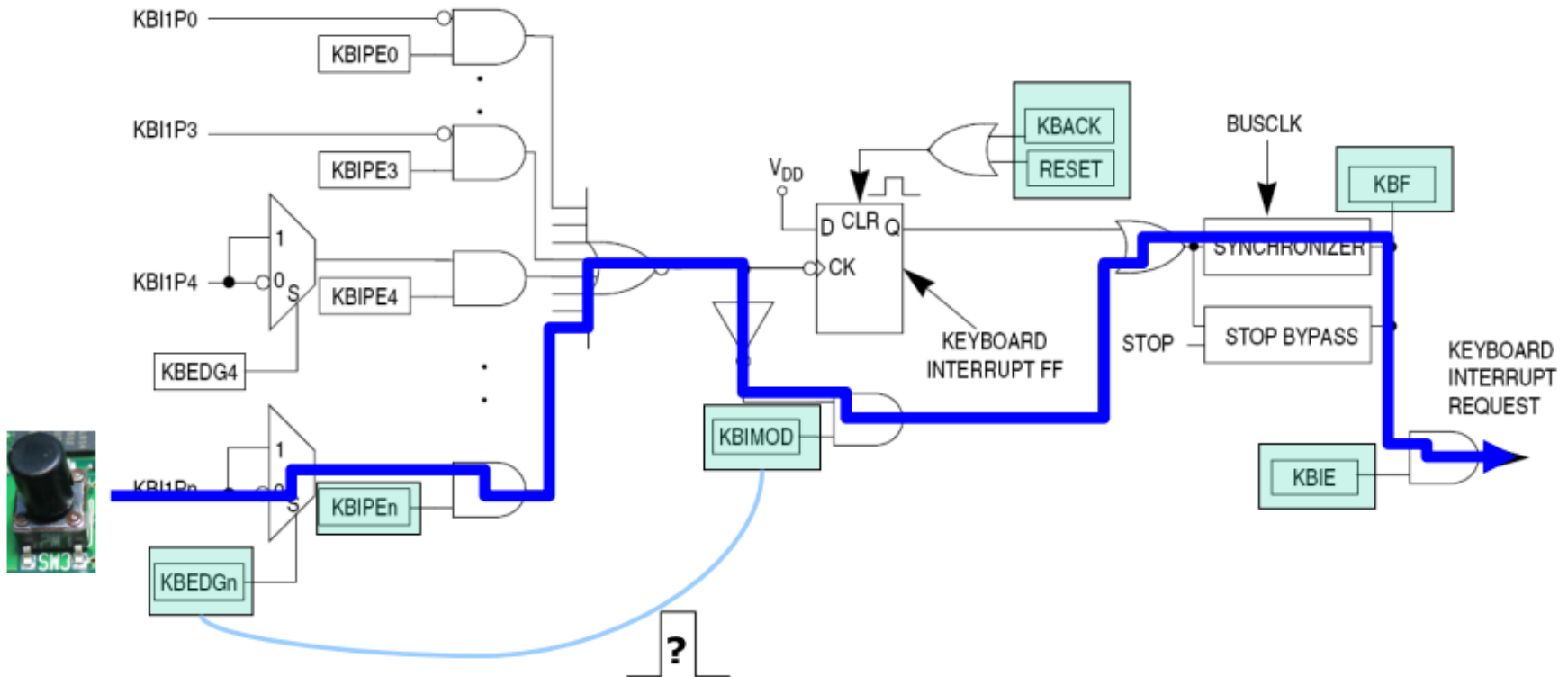

- + no Polling needed
- not sure which switch pressed

Questions

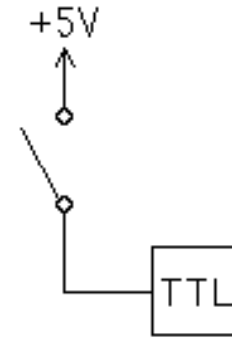1. Why is this a bad solution?
2. What is debouncing used for?
3. Pros and cons of polling?
4. Pros and cons of interrupt?



Solutions

1. No defined state if button is not pressed.
2. Nullification of the bouncing mechanical parts of a switch/button.
3. + easy programming
 - resource intensive
4. + work capacity saved for other tasks
 - sometimes not easy/possible to implement